

Intermodulation Distortion

Pete Millett

ETF.19

Agenda


- A little biography
- What is intermodulation?
- Single-ended triode amplifier transfer functions
- Two-tone waveforms and FFTs
- A special case: filament hum IMD
- Listening demo

Biography

- I've been coming to ETF since 2003
- I've been an Electrical Engineer for almost 40 years, live in Colorado, USA and work from a lab in my home
- Mostly a board level hardware guy in consumer and computers, but I've spent the last 15 years working for semiconductor companies
- Have a hobby business doing DIY audio stuff

www.pmillett.com

pmillett@hotmail.com

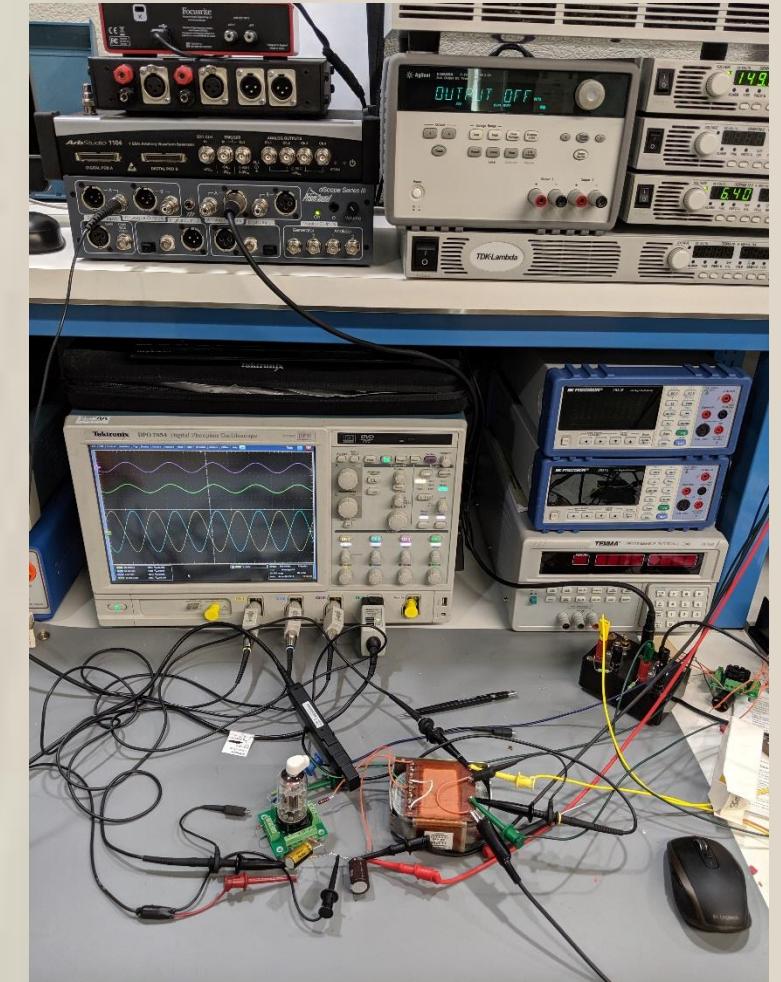

So, what is “Intermodulation Distortion”?

What is “intermodulation”?

- In an ideal circuit, if you pass two single-frequency tones in, you get only those two tones out
- Nonlinearities in a circuit cause the two signals to affect – or modulate – each other
- The result is that there are tones in the output that were not at the input
- The unwanted tones – intermodulation products – are mathematically related to the input tones

Why do we care?

- We don't usually listen to tones
- Music is a very complex signal
- However, you can imagine that the sound of one instrument might intermodulate with the sound of another
- Think of a loud bass note and a flute
- Generally IMD “muddies up” the sound or makes it sound harsh
- IMD measurement is regarded as a more telling benchmark than THD measurements

Distortion in a simple triode amplifier


A simple single-ended triode amplifier

- In a simple grounded cathode triode amplifier, the output signal is an inverted, larger version of the input signal
- Ideally,

$$V_{\text{OUT}} = -V_{\text{IN}} * A + \text{DC}$$


Where A = voltage gain, and DC = the static plate voltage (bias)

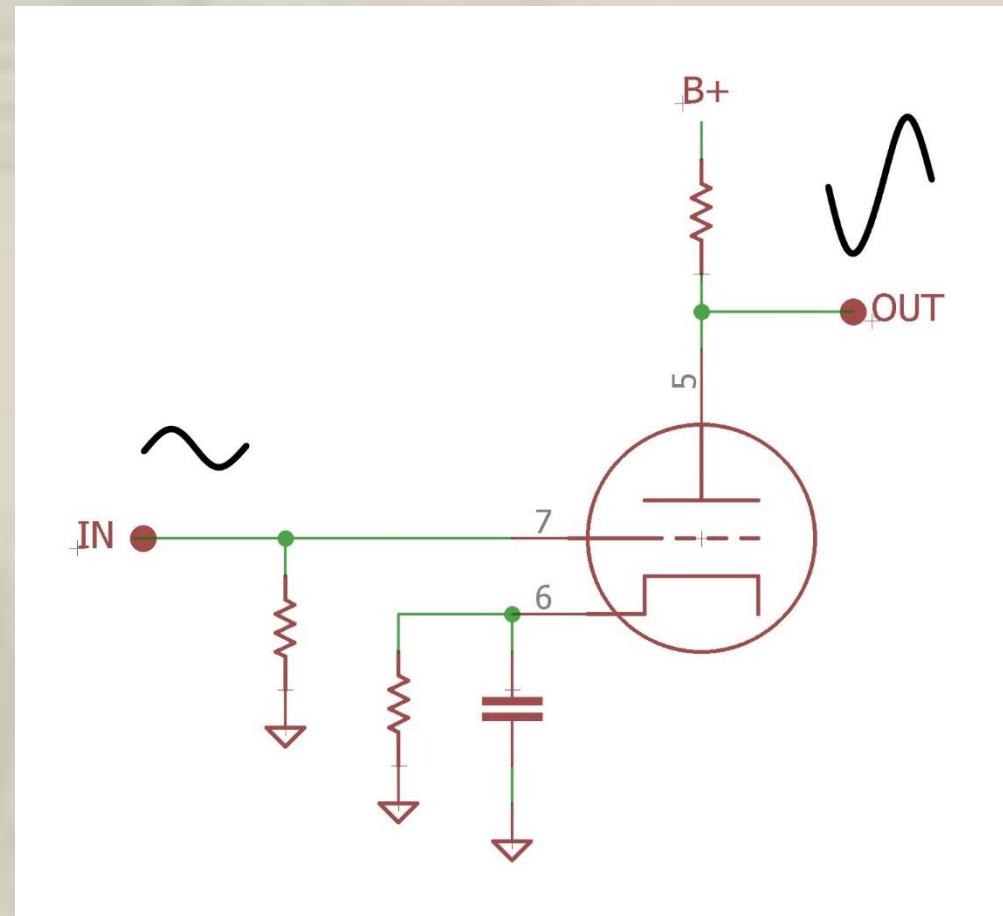- Note that this is a simple linear equation: $y = mx + b$. Remember high school algebra?





Transfer functions

- If we make a graph of an ideal amplifier's output vs. input, we get a straight line, whose slope is the gain of the amplifier
- When we talk about “nonlinearities”, it is any deviation from this straight line that we are talking about – NOT the shape of the plate curves (though they are related, as you will recognize with experience)
- You can easily construct the transfer function of a simple resistive loaded triode from the plate curves
- Linearity varies dramatically for a given triode with differing operating conditions (bias point and plate load impedance)

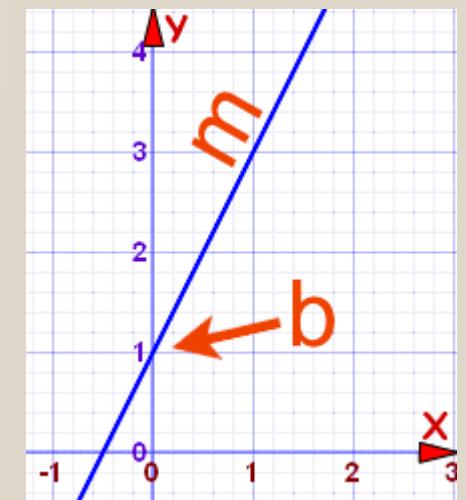

Transfer function of a real triode

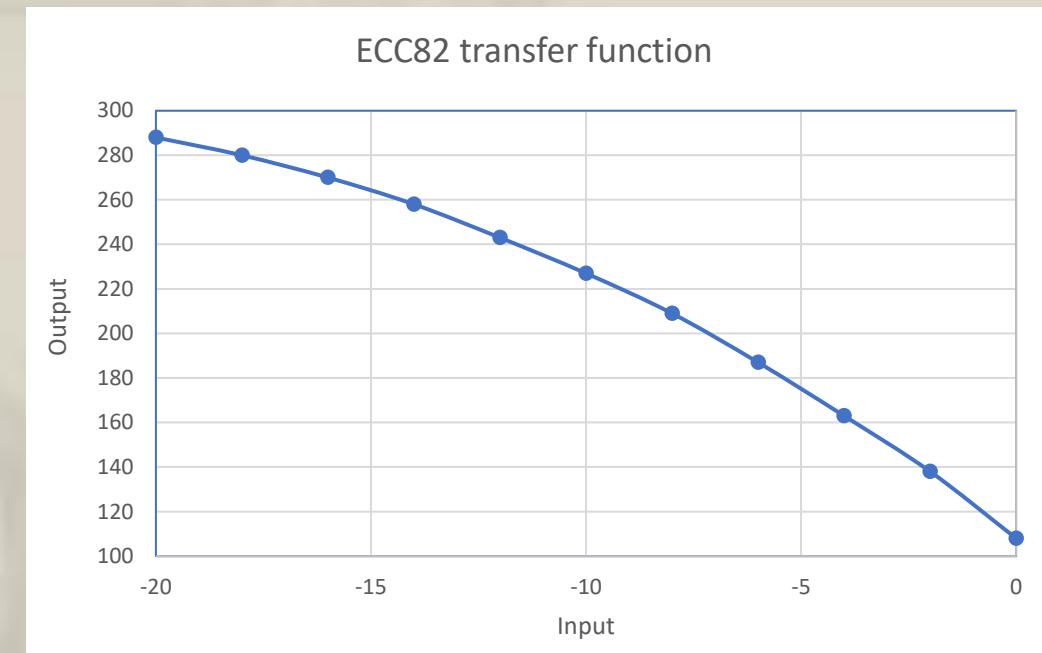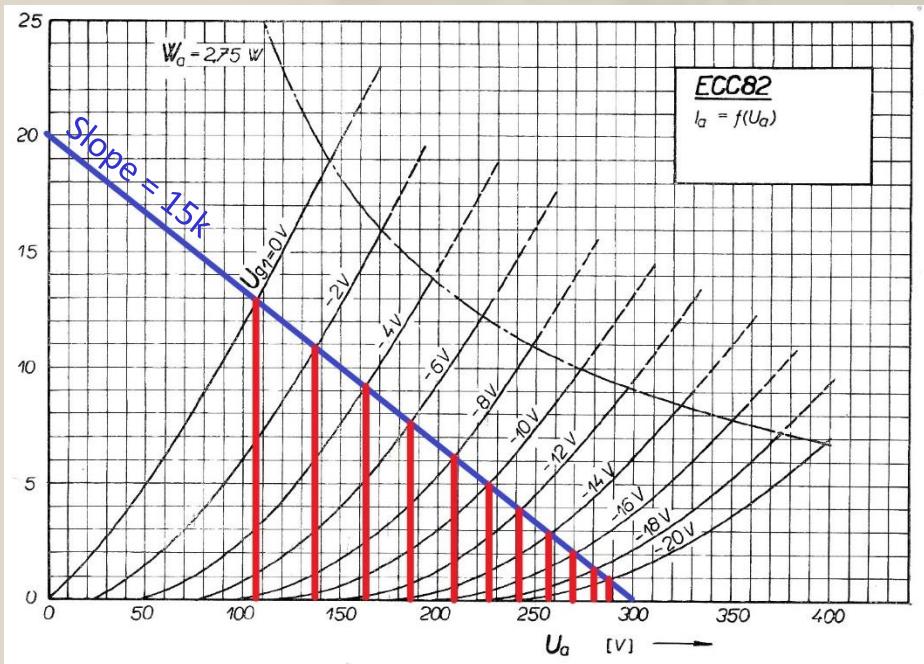
- This is an ECC82 with a 15k plate load resistor



Not a straight line! This is nonlinearity.

Single tone: harmonic distortion

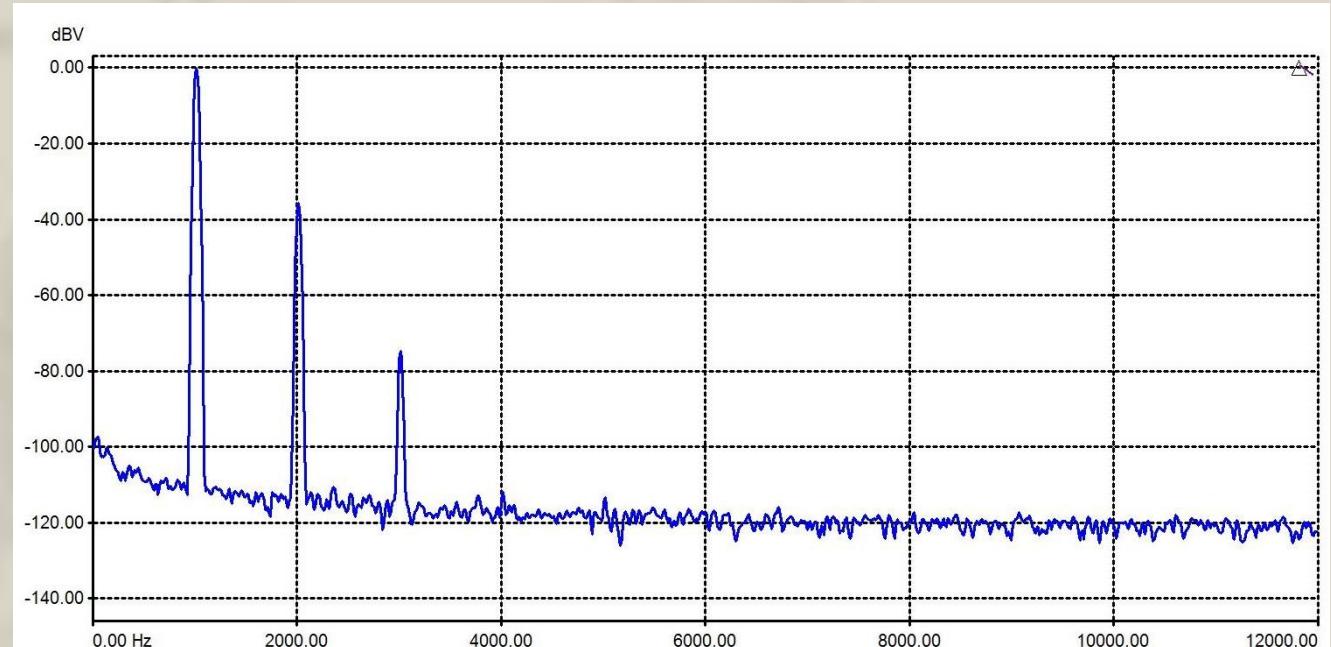
- When you apply a single frequency tone to this (not so linear) single-ended triode amplifier, you get harmonic distortion products
- An FFT (Fast Fourier Transform) plot will show the distortion products, at multiples of the input frequency
- For more on harmonic distortion and FFTs, look up my ETF.04 presentation:
http://www.pmillett.com/etf_sod.htm



Waveforms and FFTs


A bad amplifier

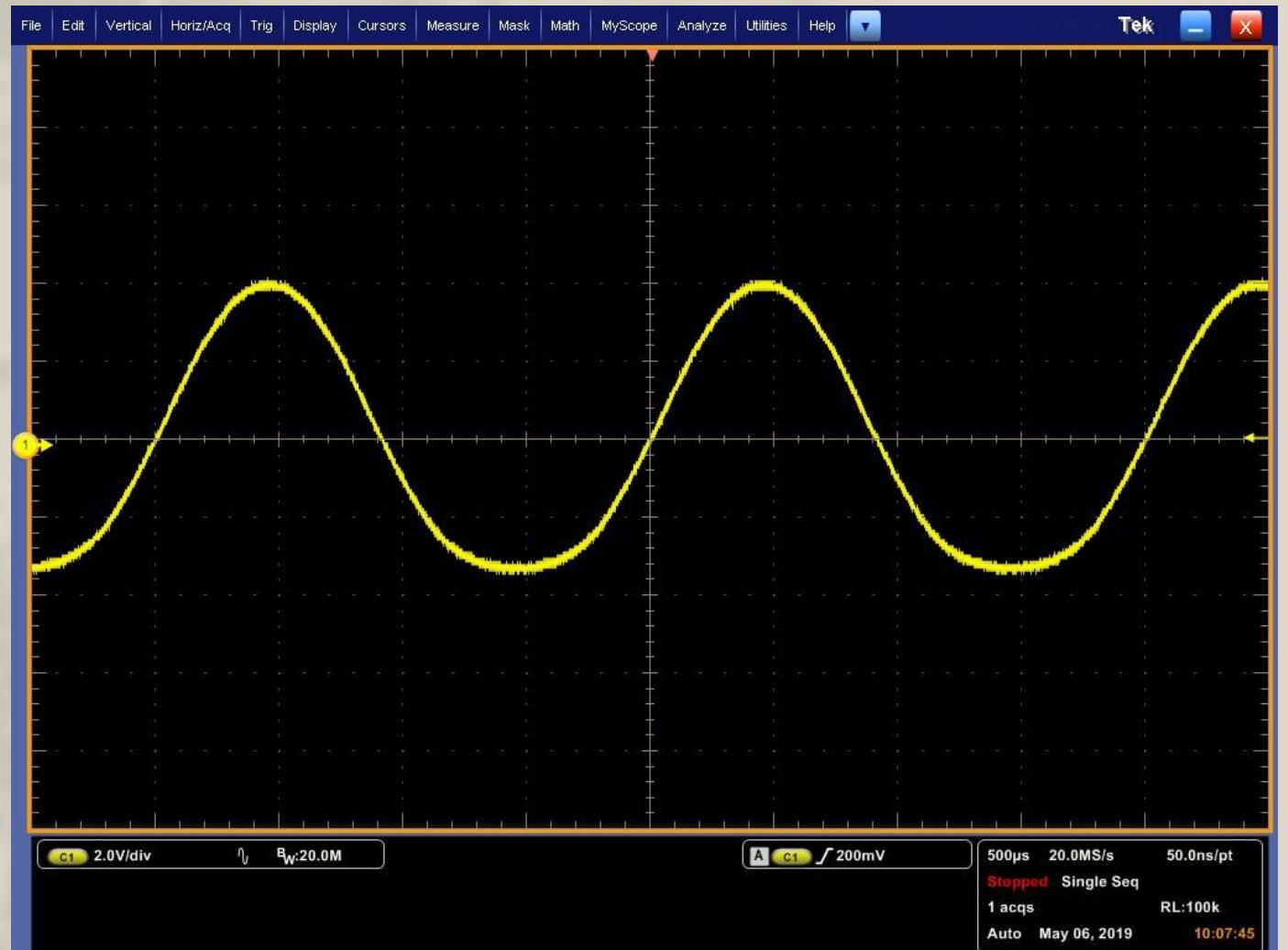- Here is an oscillosograph of the output of a particularly nonlinear amplifier, with a 400Hz input signal. You can see the asymmetry – this is mostly even order harmonic distortion.




Two tones: intermodulation

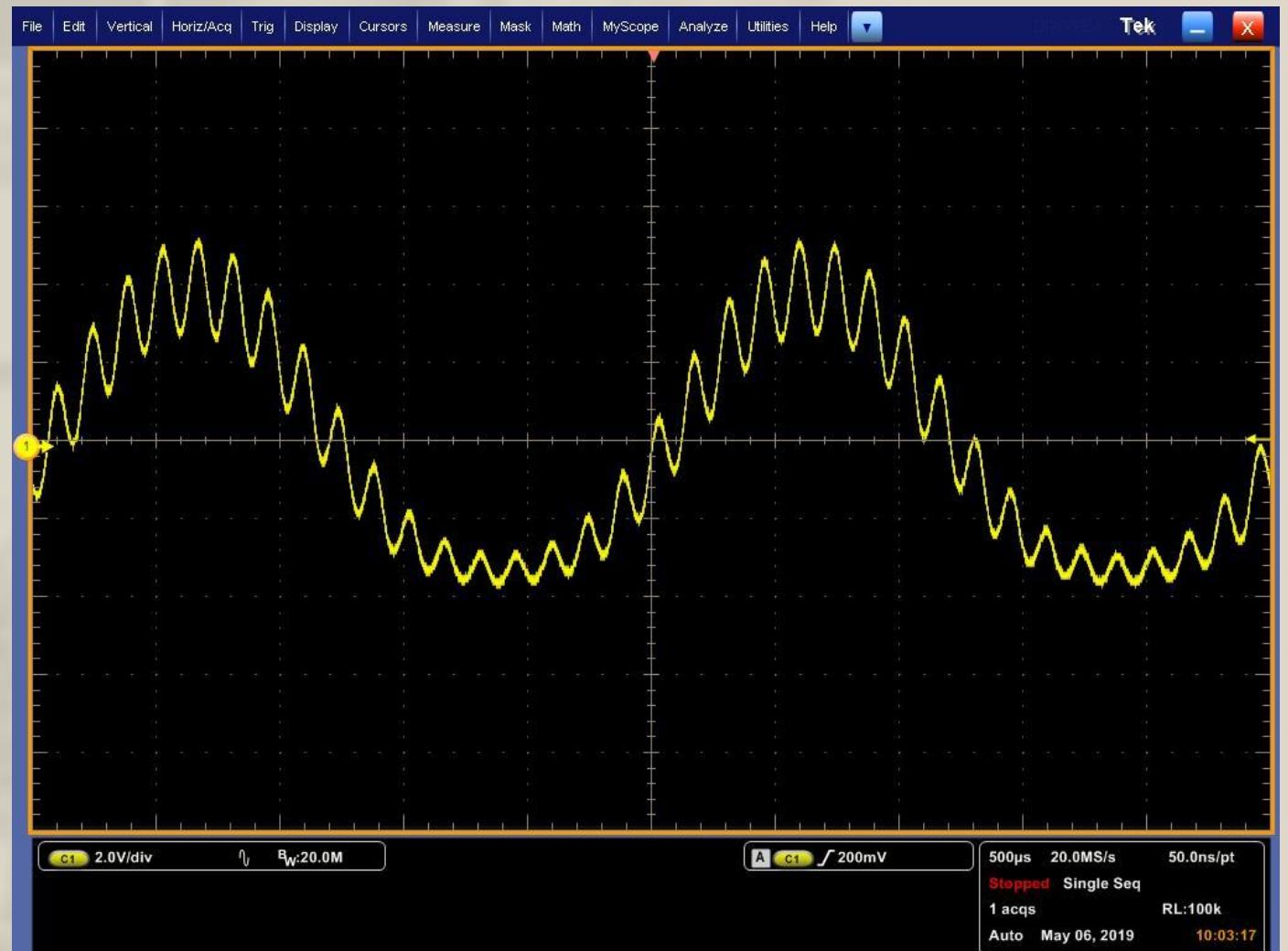- Here is an oscilloscope of a this same nonlinear amplifier, with a two tone input (400Hz and 7kHz)
- The amplitude of the HF signal varies with the LF signal
- **Any amplifier with harmonic distortion will also create IMD!**



IMD in the frequency domain (FFT)

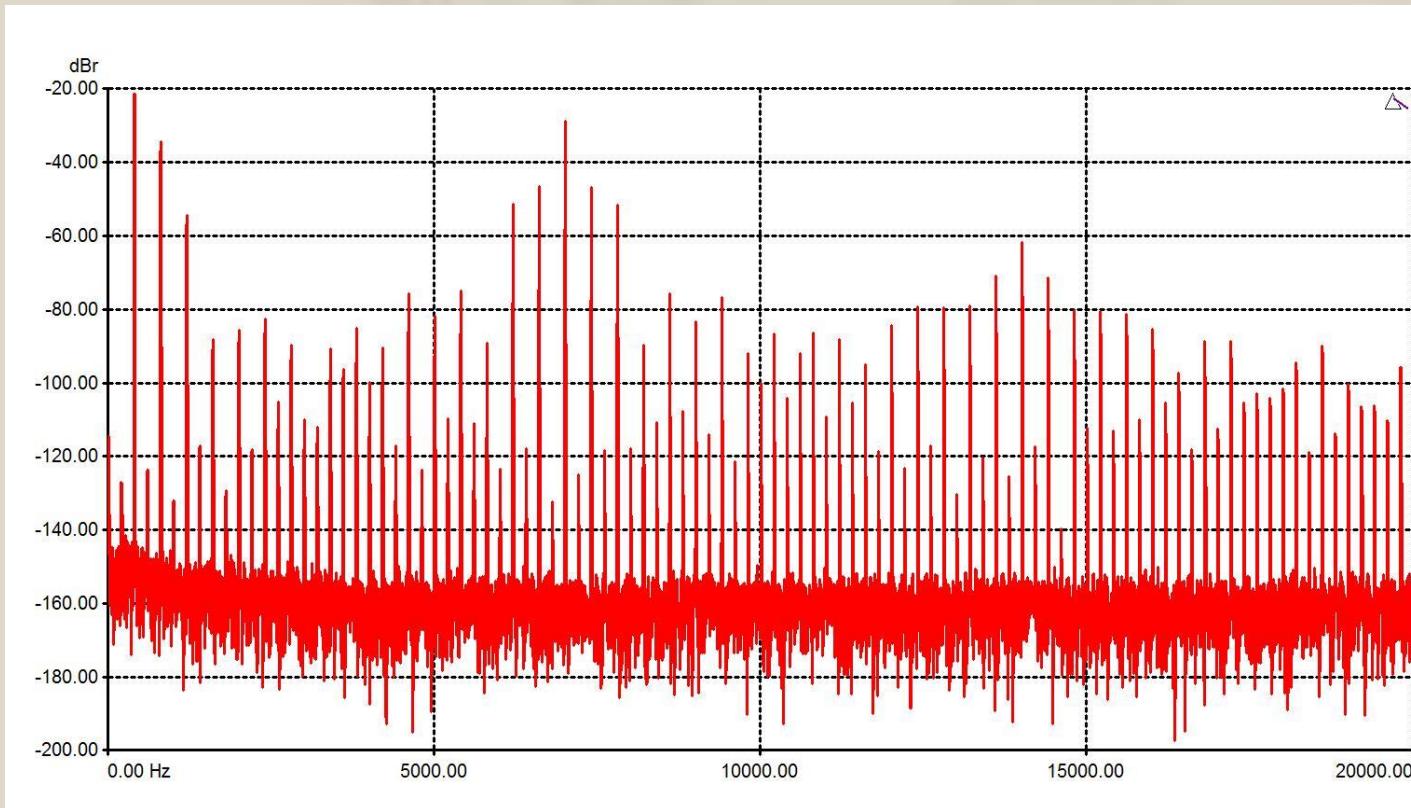
- Here is the same signal in the frequency domain (an FFT)



Not pretty!


IMD in the frequency domain (FFT)

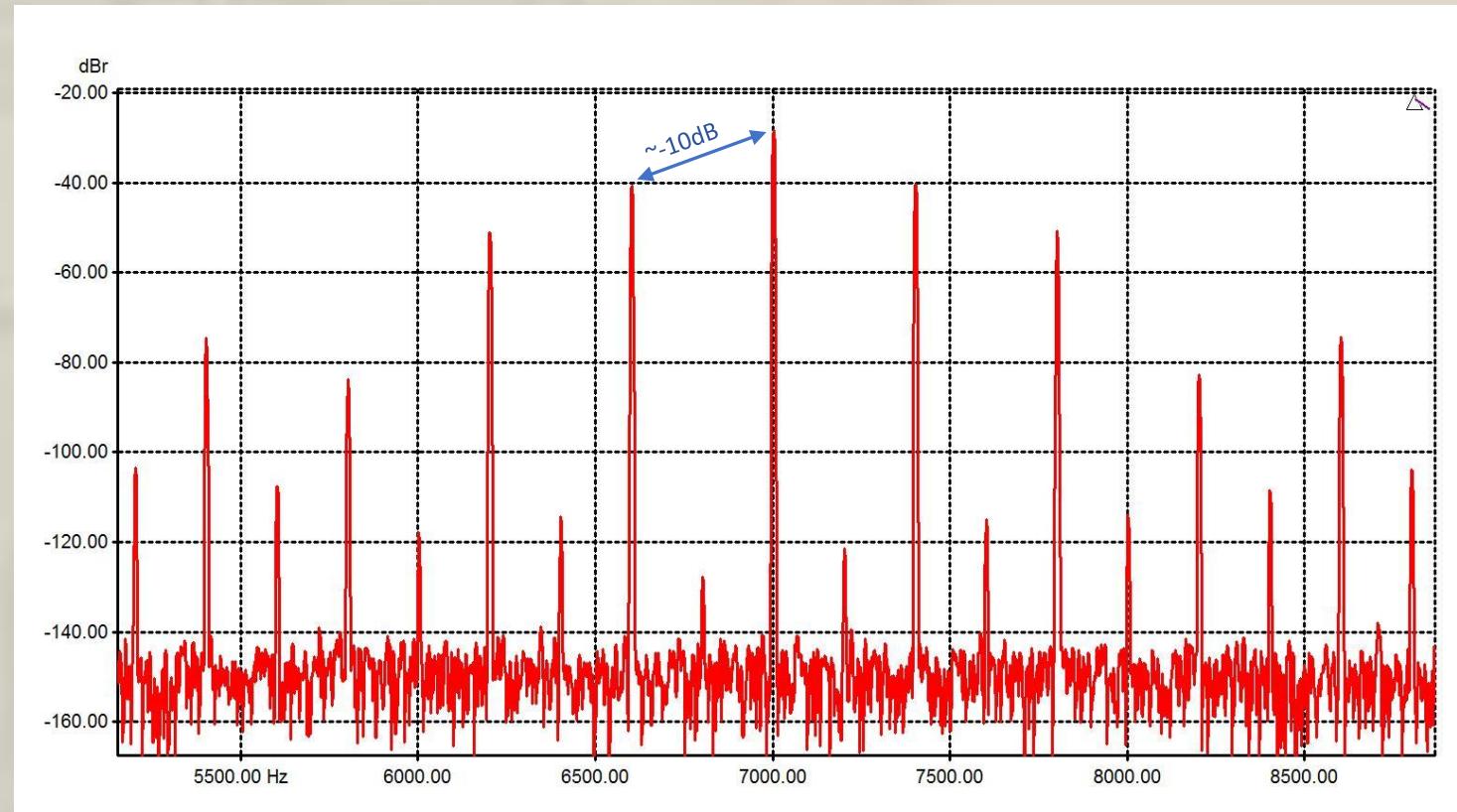- If we zoom in on the 7kHz peak, we can see peaks – sidebands – at 400Hz intervals. These signals were NOT in the input, they were generated by the nonlinearities of the amplifier. These are intermodulation products.



Effect of operating conditions on IMD

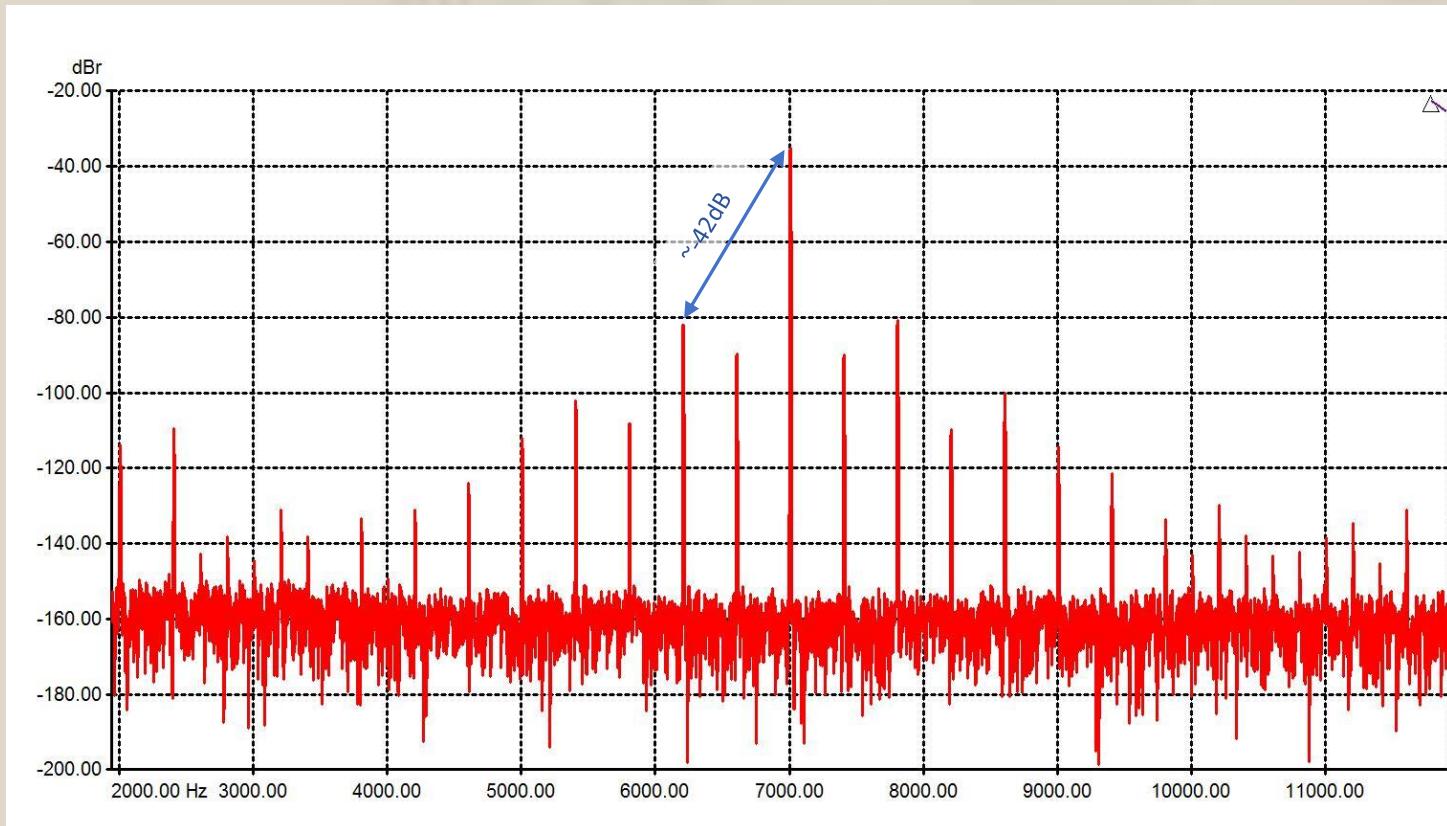
- If we re-bias this amplifier to a more linear region, things are better



Not as bad!

What we really want

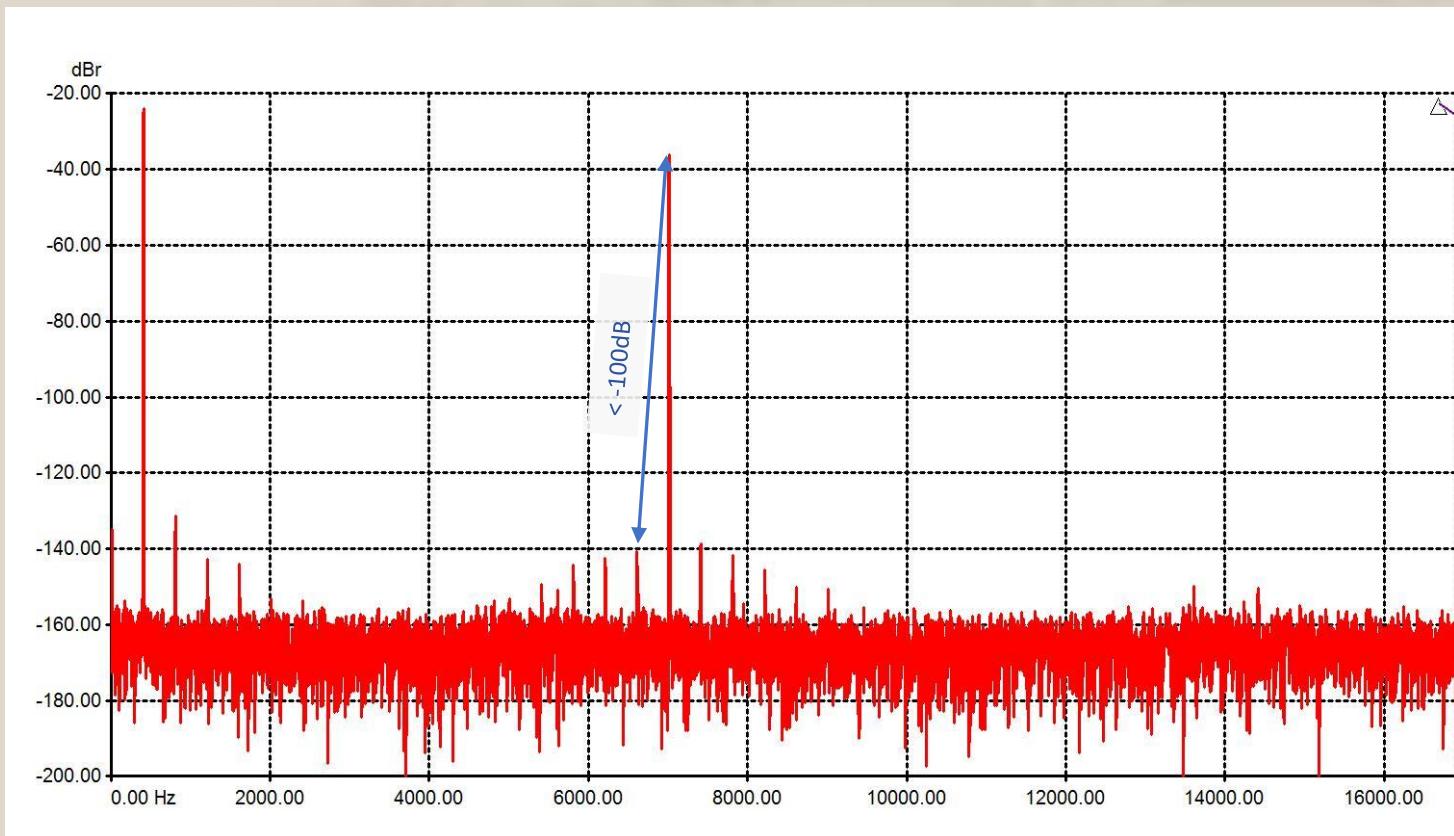- This shows what you see in an FFT with very low IMD




Cheating!

IMD measurement techniques

- Measuring IMD involves applying a two tone input signal, and measuring the amplitude of the undesired output products
- Any two tones can be used, but there are two main standards used: SMPTE and CCIF (also called DFD)
- SMPTE IMD measurements use a low amplitude high frequency signal and a high amplitude, low frequency signal, usually 7kHz and 60Hz at a 1:4 ratio, and the amplitude of 6940Hz and 7060Hz is measured
- CCIF IMD measurements use two equal amplitude high frequency signals, usually 19kHz and 20kHz, and the amplitude of the resulting 1kHz product is measured

SMpte and CCIF spectra

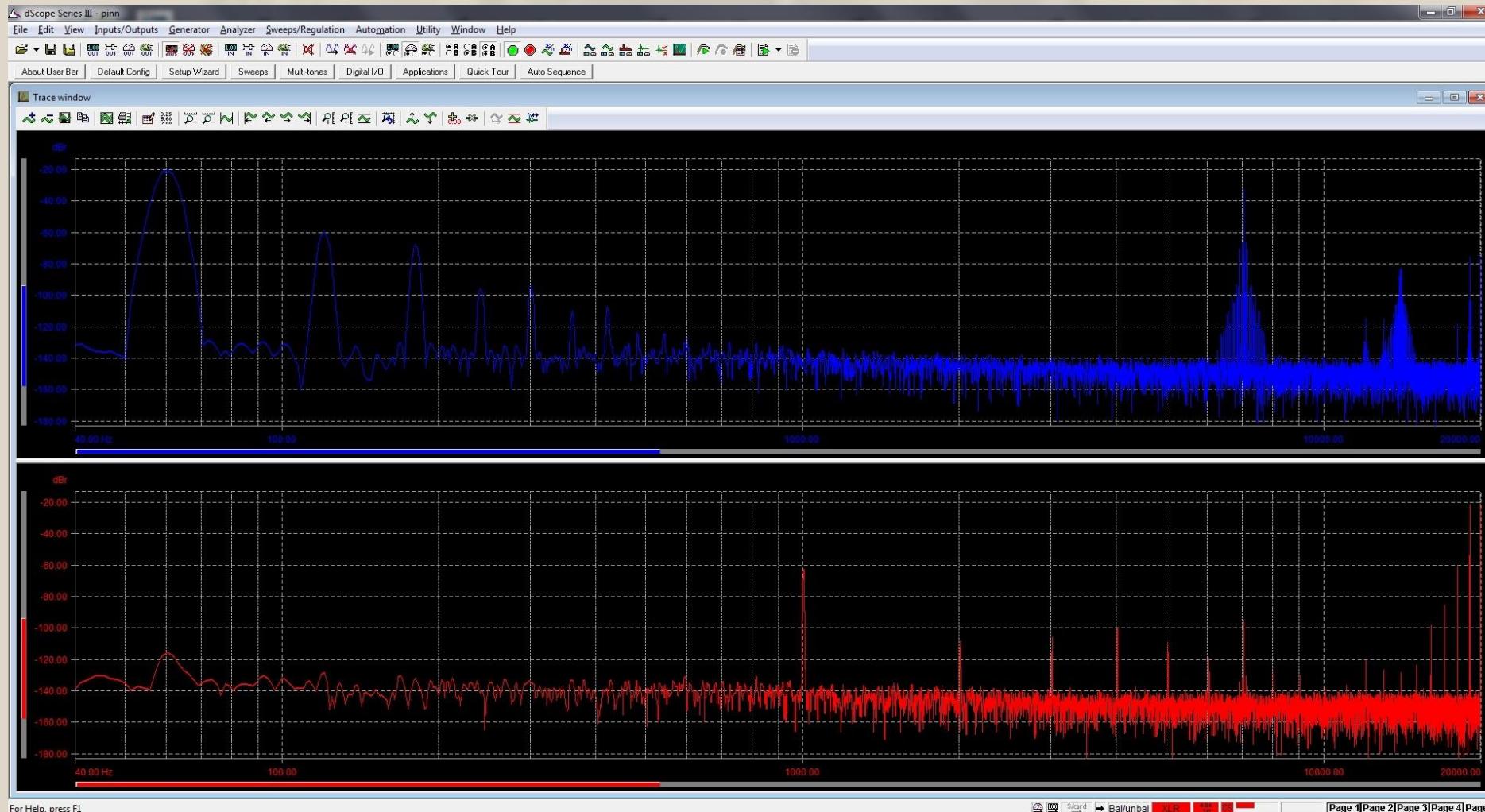


Hum Intermodulation

A special case: hum intermodulation

- “Hum intermodulation” is a phenomena that occurs in tube amplifiers
 - most severely in directly heated tube circuits when the cathode is heated with AC
- I believe there are three components of hum intermodulation: thermal modulation, filament asymmetry-related modulation, and IMD that is produced from hum coupled into the audio path
- Note that ripple on B+ will also intermodulate with the signal
- Reference works of Steph Bench and Dmitry Nizhegorodov:
 - <http://diyaudioprojects.com/mirror/members.aol.com/sbench/humbal.html>
 - <http://www.dmitrynizh.com/filament-ac-freq.htm>
 - <http://www.dmitrynizh.com/filament-ac-harmonic.htm>


US Patent #2,078,666 – 1937 – The IDHT

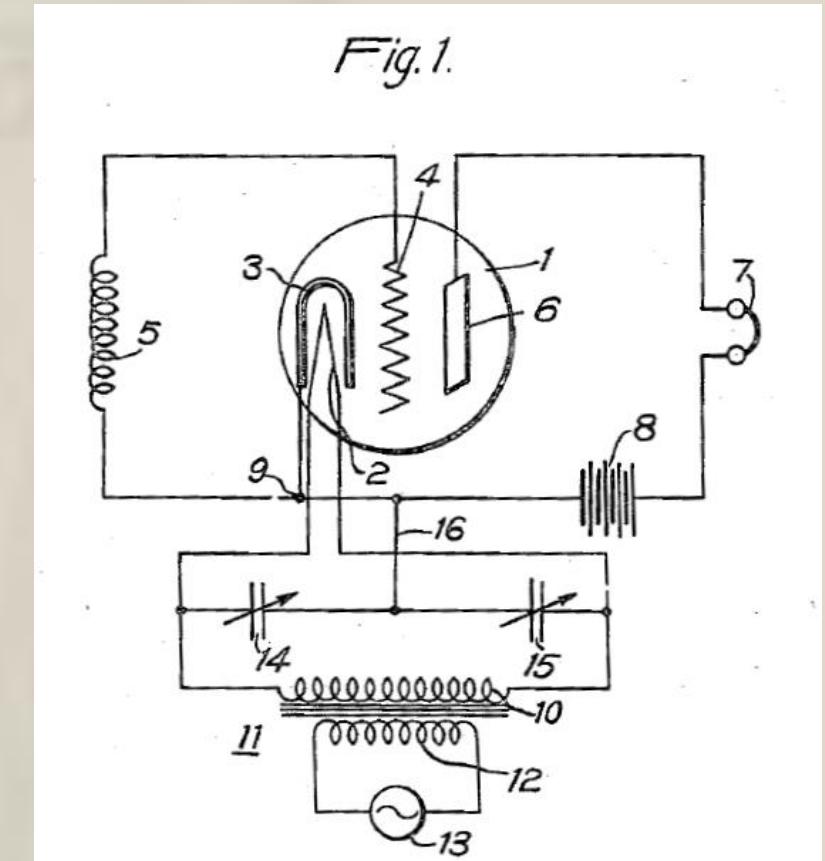“The hum is due, in part, to the variation in temperature of the electron-emitting means and, in part, to modulation of the space current by the magnetic field surrounding the heater element. The hum is also due, to a great extent, to variations in the potential of both grid and plate with reference to the thermionic emitting element or cathode.”




Thermal modulation

- When heated with AC, a filament is actually heating and cooling at twice the applied frequency. However, this effect isn't that big...
- The gain of a triode amplifier varies with the triode's transconductance, which varies with cathode emission. It is essentially non-existent with indirectly heated tubes.
- When heated with AC, a filament has small changes of emission at double the AC heating frequency, as the filament heats and cools

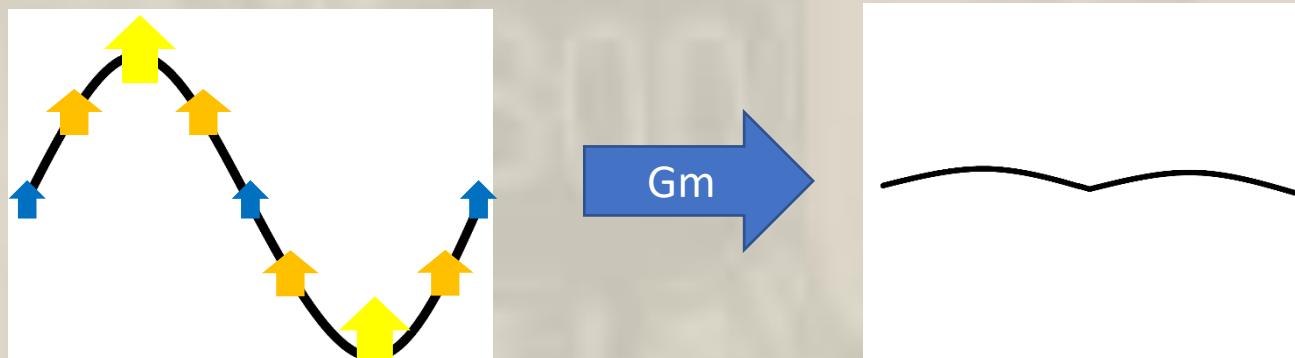


Filament emission

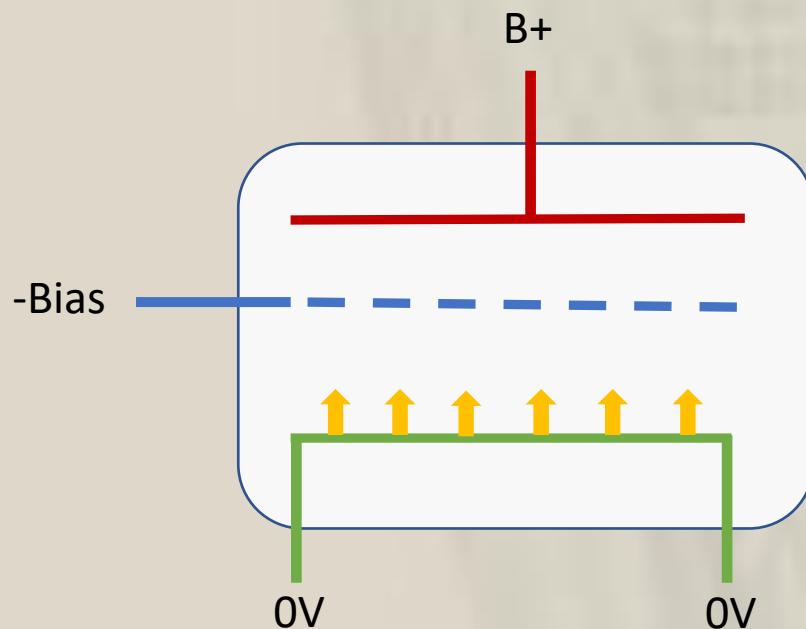

- When the filament is heated with AC, twice per cycle, both ends of the filament are at 0V (or at least at the same DC voltage)
- At this time, the voltage difference between every point on the filament and grid is equal

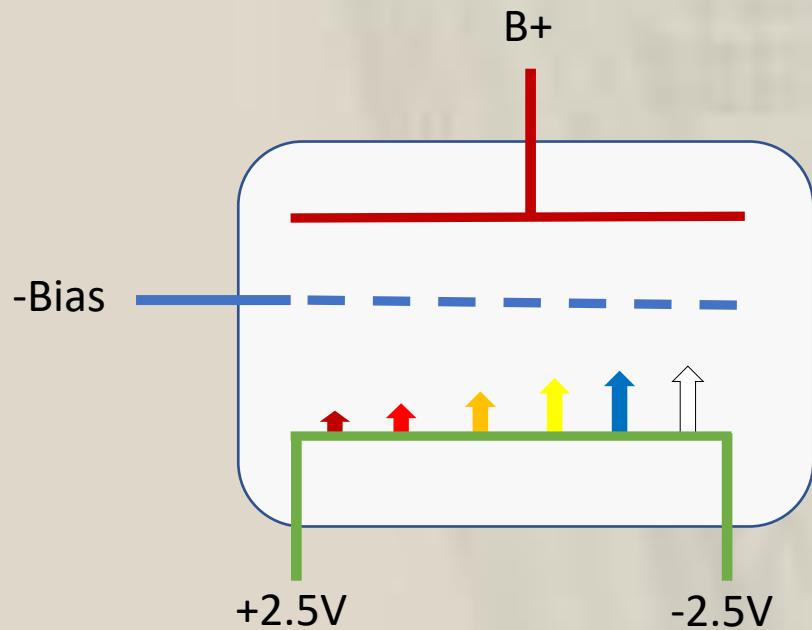
Filament voltage influences effective bias




- As the voltage applied to the filament changes, so does the *relative* voltage between each part of the filament and the grid
- Effectively, the bias voltage is now different at different points on the filament, and one end emits more electrons than the other
- If the tube were perfect, the *average* grid-filament voltage should be the same throughout the AC cycle – and there would then be no hum from this

Tubes are imperfect!

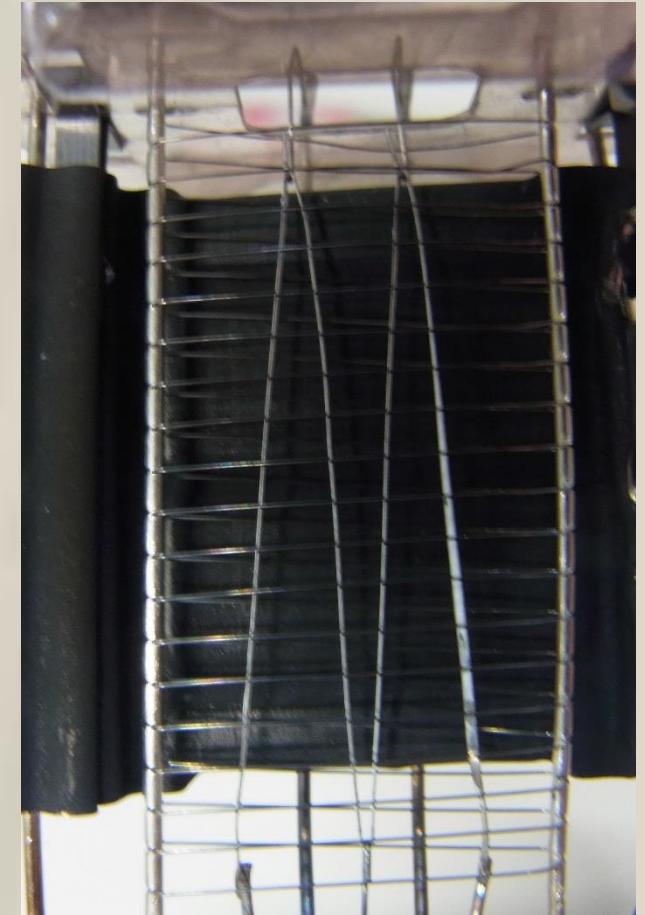- A real directly heated triode is far from perfectly constructed!
- Filaments are often not symmetrical top-to-bottom and not perfectly centered within the grid structure
- Some grid wires may be closer or farther from the filament on one end
- Emissivity may vary from one end of the filament to the other



The result: intermodulation

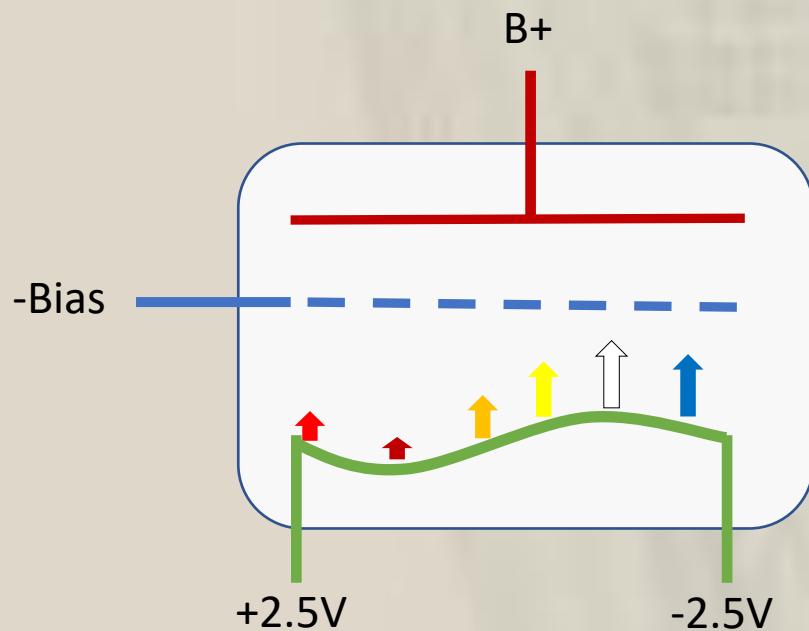


- Asymmetries result in varying emission at different points in the AC waveform
- The result is varying gm at different points in the waveform
- As before, this gm variation modulates the desired signal

Coupled-hum IMD

- Any line frequency interference that is coupled into the audio path will also intermodulate with the desired signal, due to harmonic distortion in the amplifier
- Coupling can be capacitive – like AC mains wiring run next to signal wiring – or magnetic, especially between power supply transformers or chokes and input or interstage transformers
- Ripple on B+ also causes this
- This is probably the main form of hum IMD in indirectly heated tube circuits?

Harmonic distortion induced hum IMD

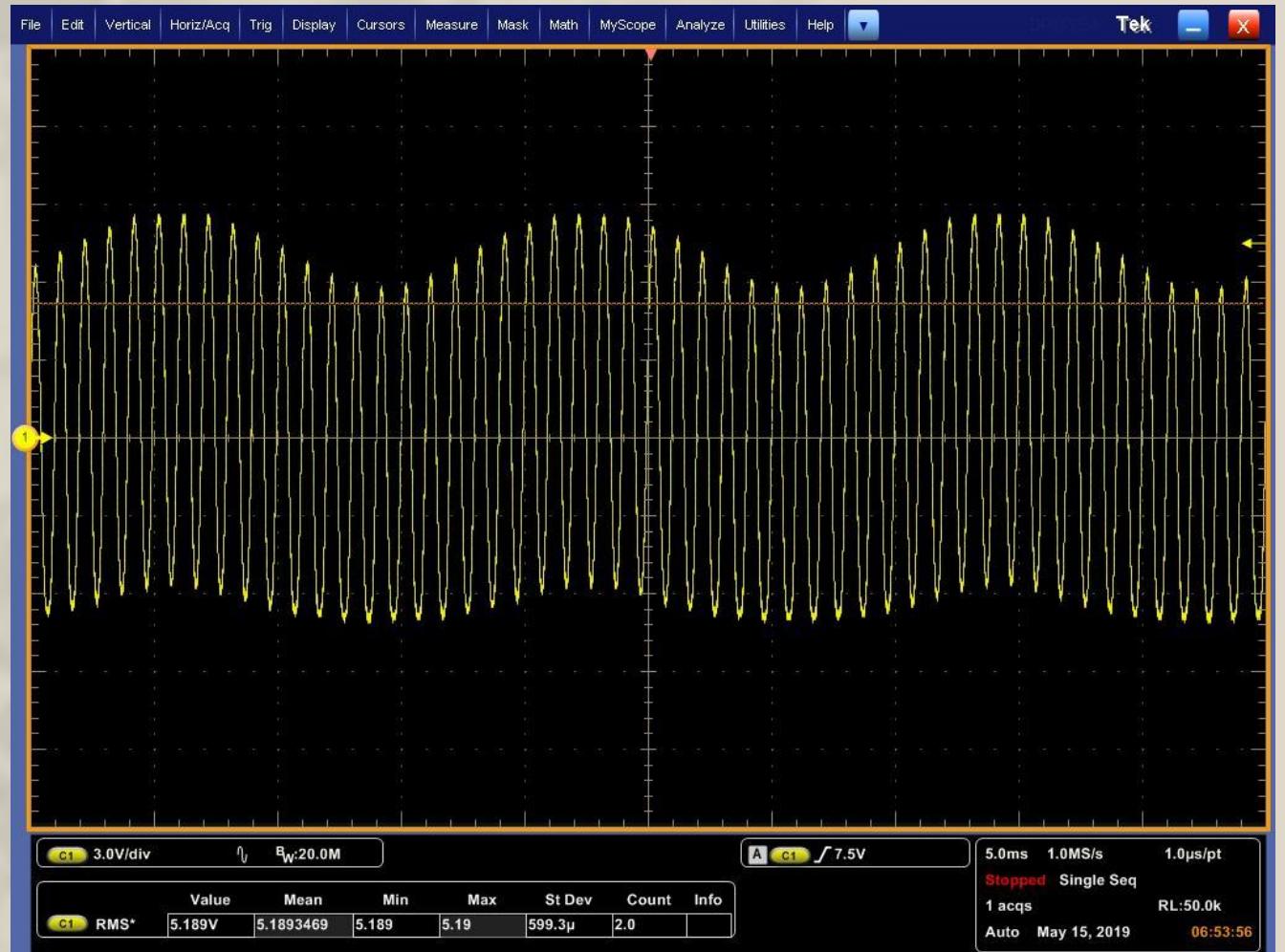- You can see the effect here. This shows a 1kHz signal with a huge amount of 60Hz hum.
- The amplitude of the 1kHz signal is being modulated by the 60Hz signal.






Let's hear this distortion...


Listening demonstration

- I built a circuit to demonstrate IMD - especially hum IMD
- I hoped to be able to demonstrate this using a real triode, but the effects are too subtle. So I built a circuit that can generate extreme levels of IMD.
- The circuit uses multiplier ICs to amplitude modulate the music signal with an adjustable sine wave signal
- This generates pure IMD – and very little harmonic distortion


The “IMD Modulator”

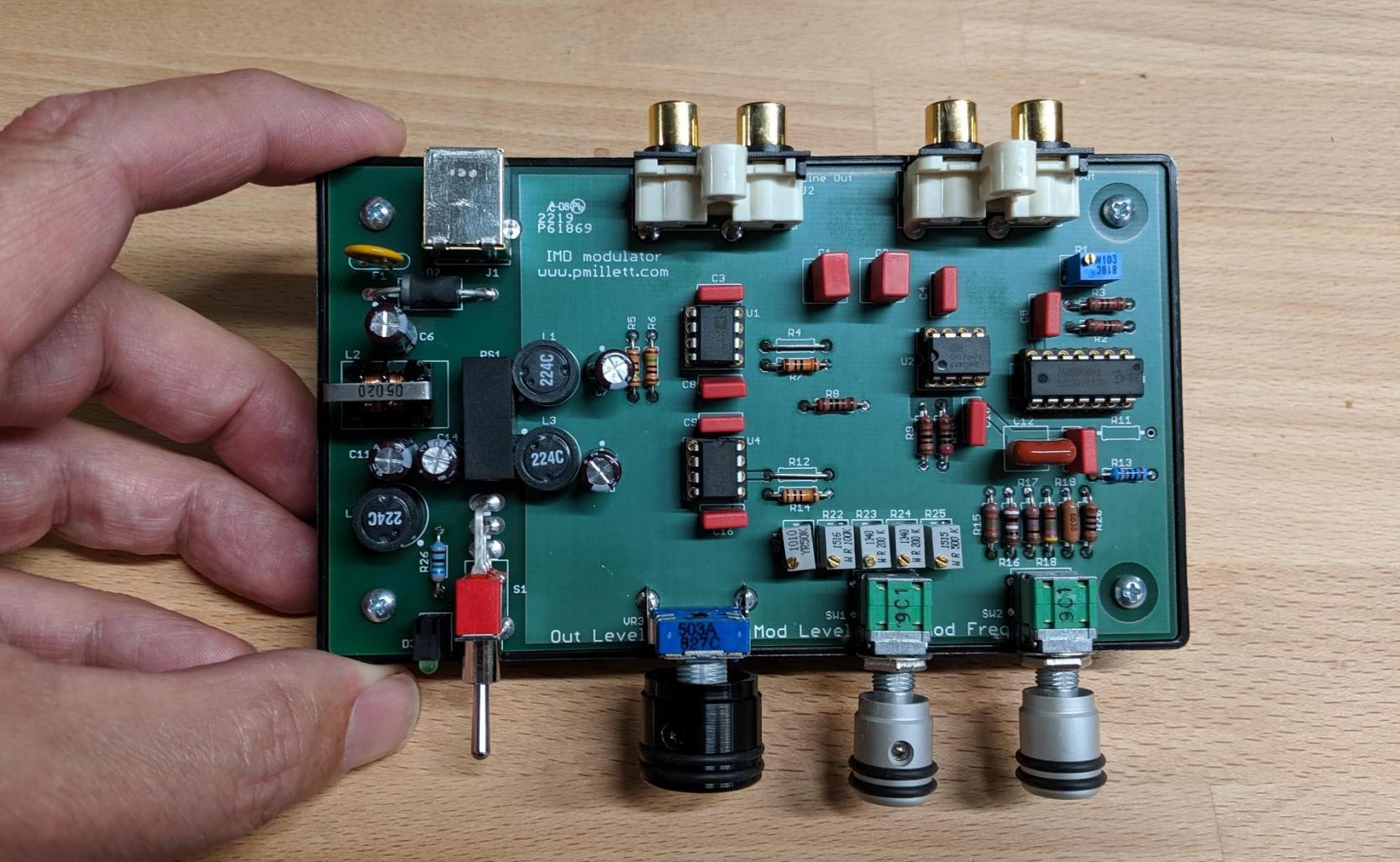


The circuit - Modulator

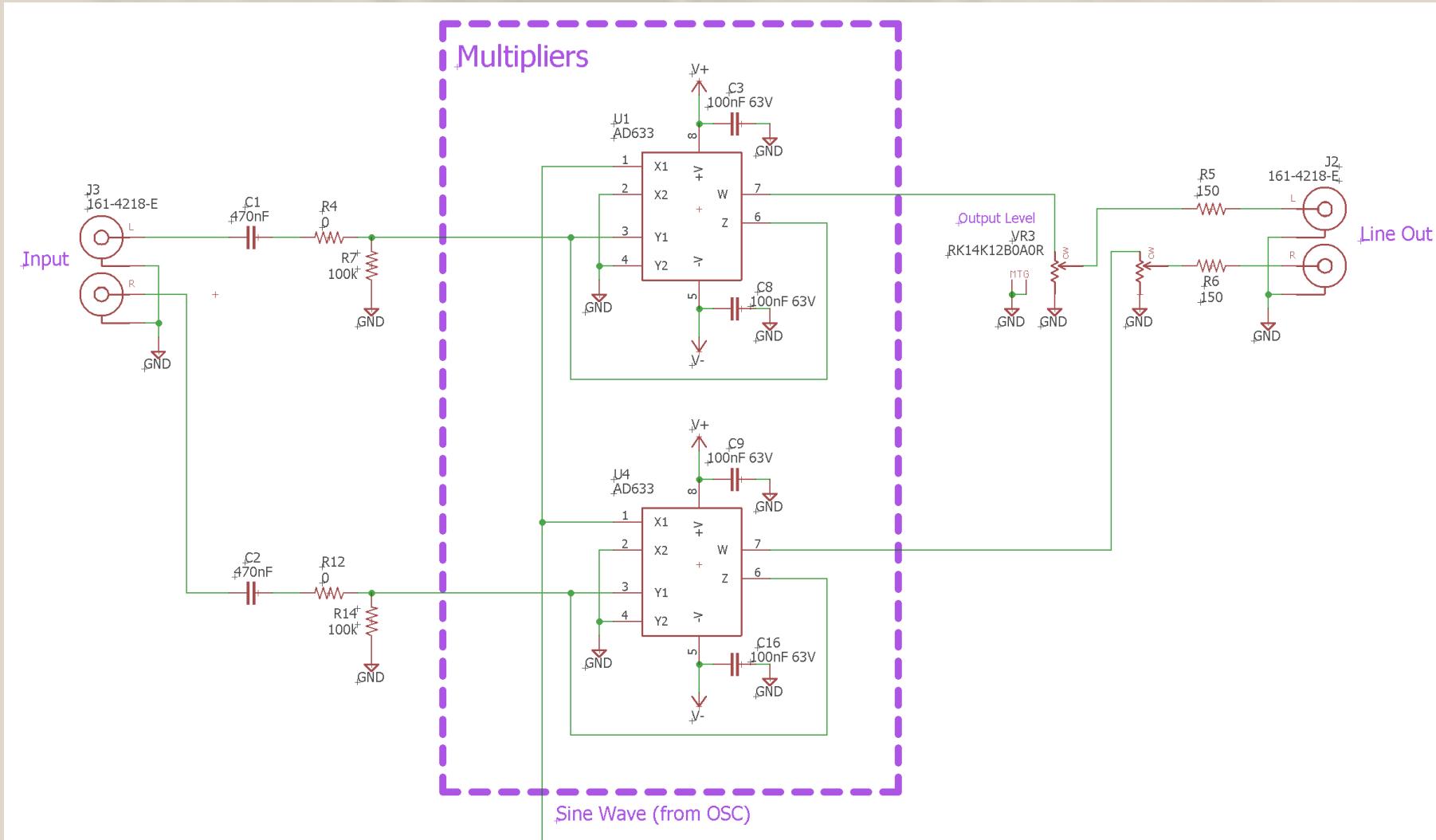

The circuit – Sine Oscillator

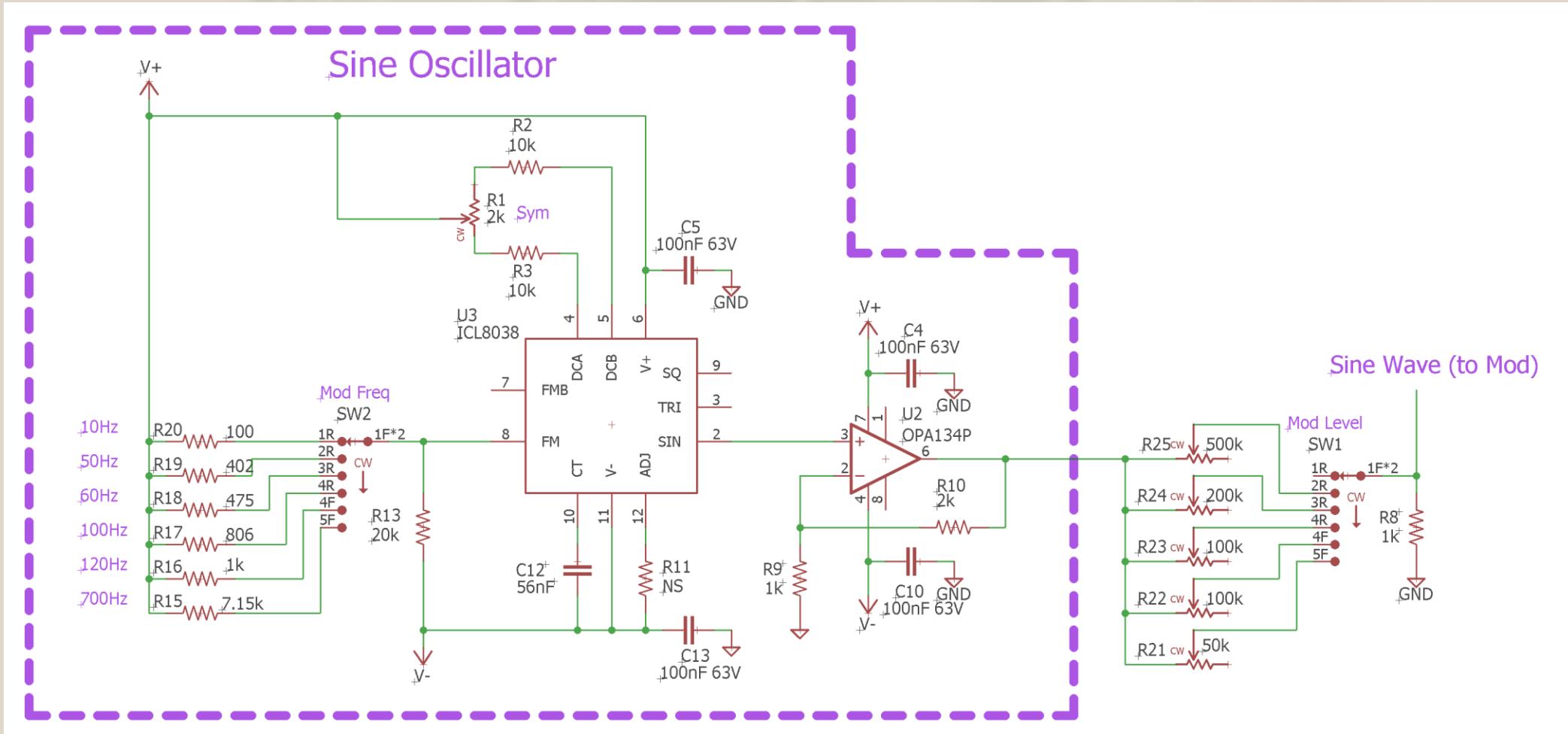

The circuit – Power Supply

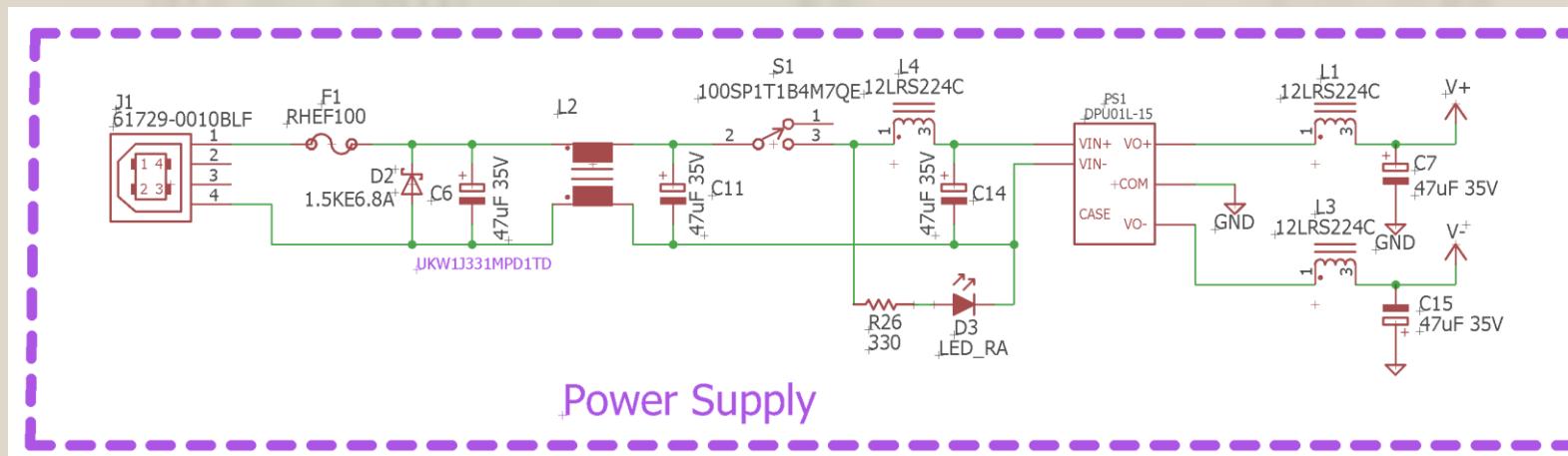

Settings

- The IMD modulator has two adjustments: Oscillator frequency, and modulation depth (as well as an output volume control)
- The frequency is selectable around normal line frequencies (and 2x those frequencies), as well as one low frequency (around 10Hz) and one high (around 700Hz)
- The modulation level (level of the first sideband) can be adjusted between none and -8dB, which is 50% IMD
- I'll use audio generated from my laptop via a USB DAC for the demo

Listening to Sine Waves?

- Most of us don't spend a lot of time listening to sine waves. OK, some of us nut cases might...
- IMD is easily heard on a sine wave, so...
- We will start with a sine wave



Music

- So now we'll try some music...
- I was surprised that some types of music that I expected to be less... annoying... with IMD added were not as easy to distinguish as I thought
- If it's bad enough obviously you can hear it on anything

That's it...

- Questions?
- Comments?

